

1. Compute the current through the load  $R_L = 2\text{ k}\Omega$  and the diode D by assuming Si diode with cut-in voltage of 0.7

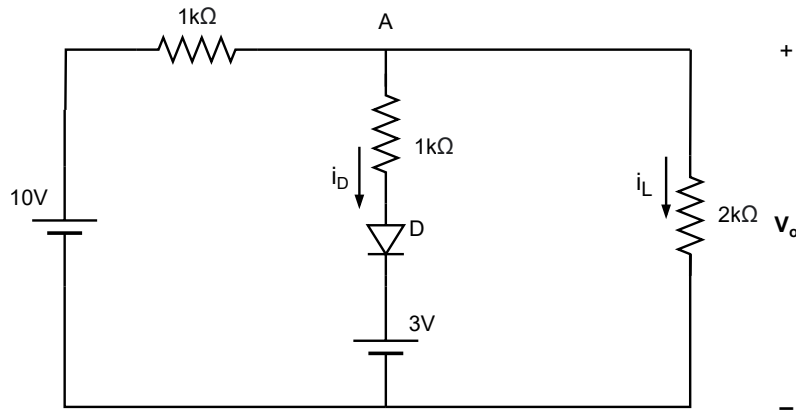


Figure 1

**Solution:**

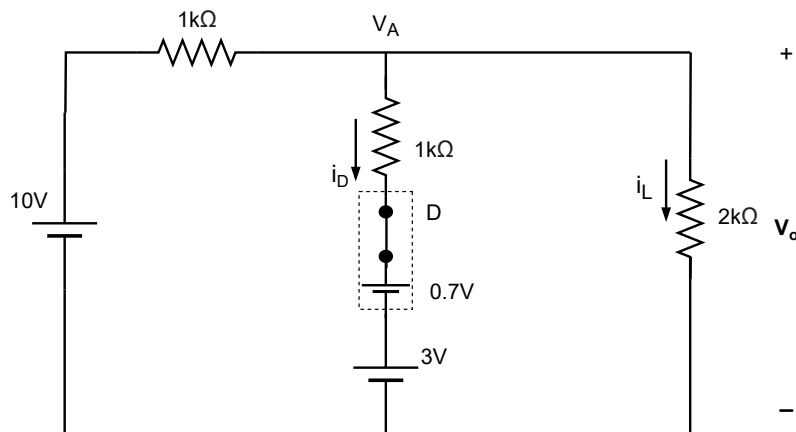


Figure 2

Applying KCL at node A

$$\begin{aligned}\frac{10 - V_A}{1} &= \frac{V_A - 3.7}{1} + \frac{V_A}{2} \\ 10 - V_A &= V_A - 3.7 + \frac{V_A}{2} \\ \frac{5V_A}{2} &= 13.7 \\ V_A &= 5.48\text{V}\end{aligned}$$

$$i_L = \frac{V_A}{R_L} = \frac{5.48\text{V}}{2\text{k}\Omega} = 2.74\text{ mA}$$

$$i_D = \frac{5.48 - 3.7}{1\text{k}\Omega} = 1.78\text{ mA}$$

2. Compute the minimum voltage required to turn the diode D "ON". Accordingly, find the transfer function (output  $V_o$  as a function of input  $v_i$ )

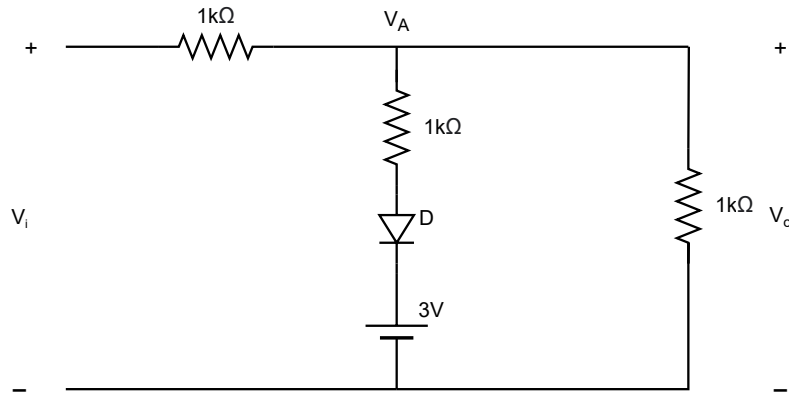


Figure 3

**Solution:**

$$V_i - V_A = V_A - 3.7 + V_A$$

$$V_i + 3.7 = 3V_A$$

$$V_A = \frac{1}{3}(V_i + 3.7)$$

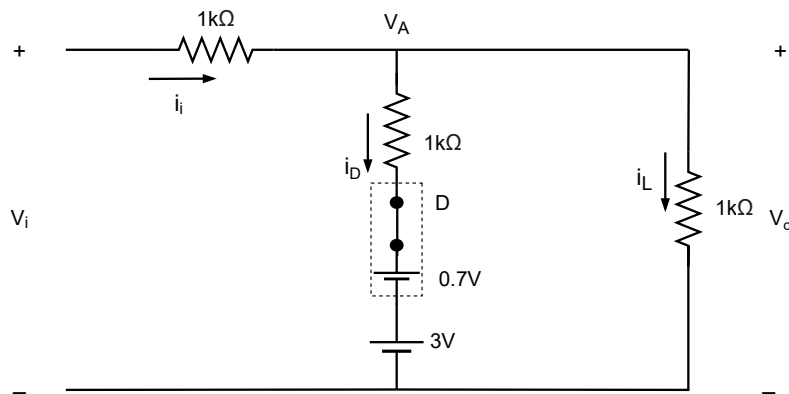


Figure 4

For the diode D to be On, we require

$$V_A \geq 3.7$$

$$\Rightarrow \frac{1}{3}(V_i + 3.7) \geq 3.7$$

$$V_i \geq 7.4V$$

The transfer function is given as

$$V_o = V_A$$

$$V_o = \frac{1}{3}(V_i + 3.7) \quad \text{for } V_i \geq 7.4V$$

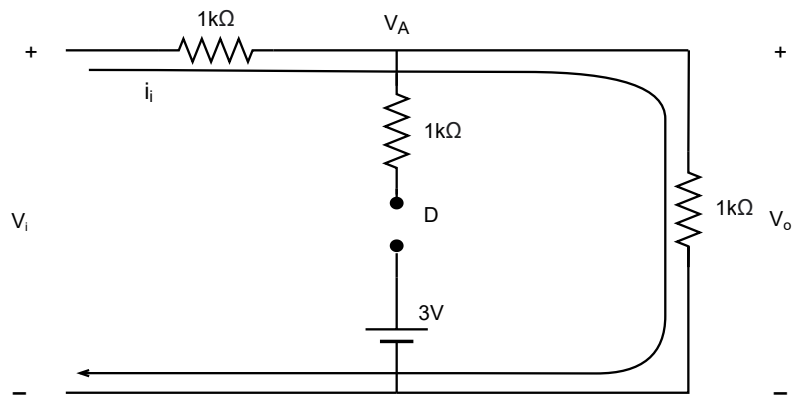


Figure 5

For  $V_i \leq 7.4V$ , diode D is reverse biased; the transfer function is given by

$$V_o = \frac{V_i}{2} \quad \text{for } V_i \leq 7.4V$$

Hence,

$$V_o = \begin{cases} \frac{V_i}{2} & V_i \leq 7.4V \\ \frac{1}{3}(V_i + 3.7) & V_i \geq 7.4V \end{cases}$$

3. Assuming diodes to be ideal, determine the transfer function characteristics of the circuit

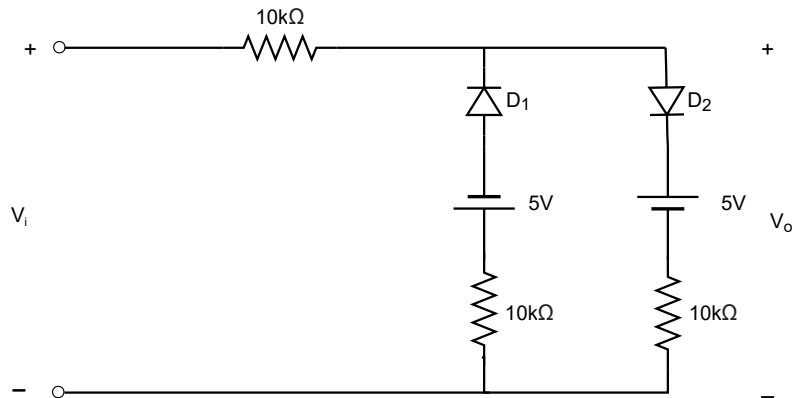


Figure 6

### Solution

Case 1

$$V_i \leq -5V$$

$$D_1 \quad - \quad \text{On} \quad ; \quad D_2 \quad - \quad \text{Off}$$

$$V_o = V_i \frac{10}{10 + 10} - 5 \frac{10}{10 + 10}$$

$$V_o = 0.5V_i - 2.5$$

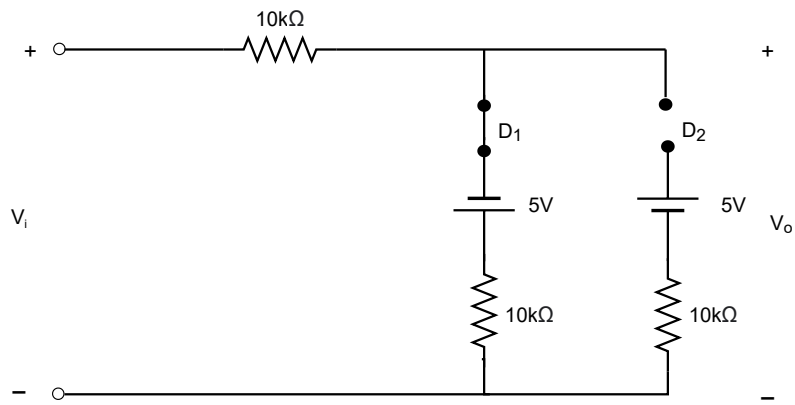


Figure 7

Case 2

$$V_i \geq 5V$$

$$D_1 - Off ; D_2 - On$$

$$V_o = V_i \frac{10}{10 + 10} + 5 \frac{10}{10 + 10}$$

$$V_o = 0.5V_i + 2.5$$

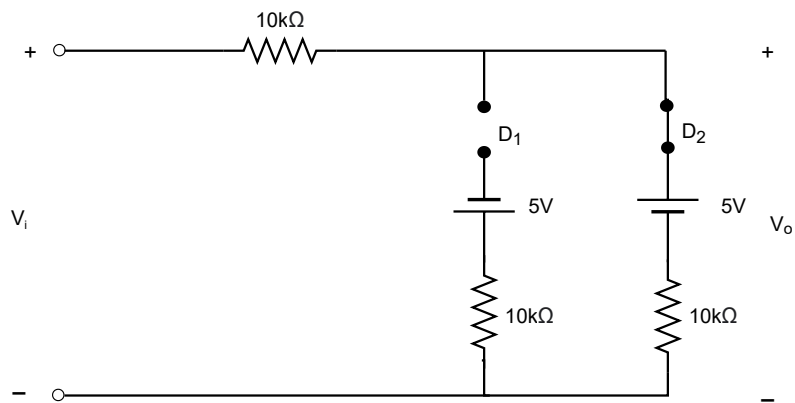


Figure 8

Case 3

$$-5 \leq V_i \leq 5V$$

$$Both D_1 and D_2 - Off$$

$$V_o = V_i$$

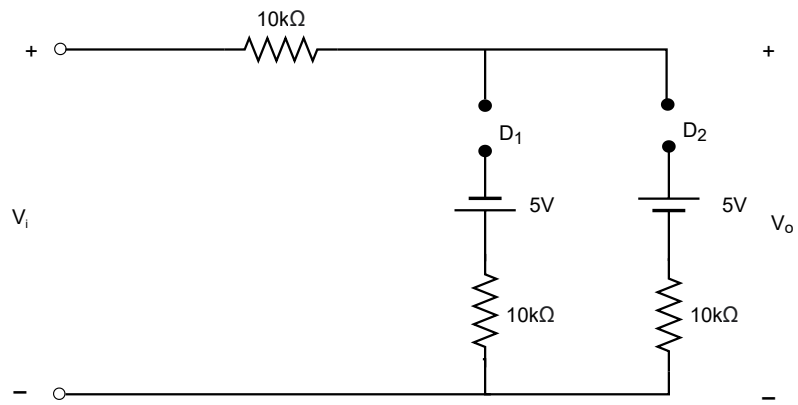


Figure 9

This is represented graphically as

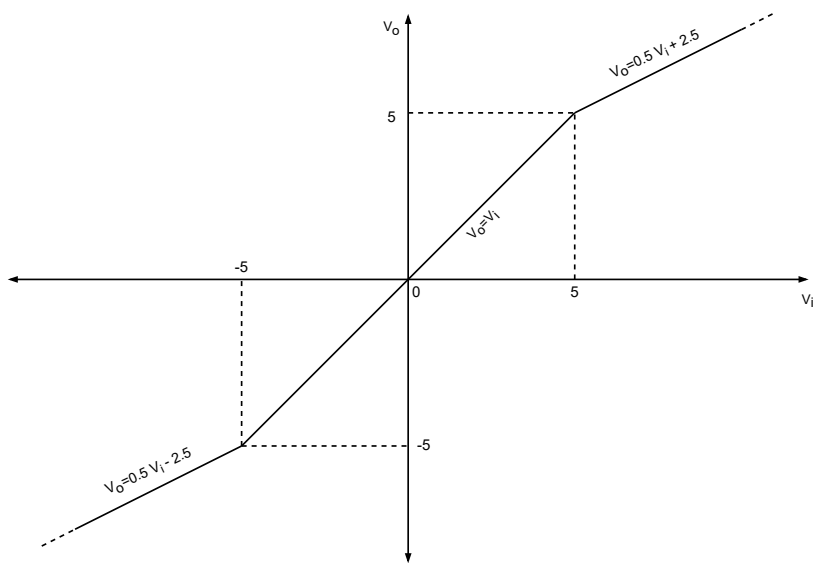


Figure 10

4. Calculate the line currents in the three-wire  $Y - Y$  system of Figure 11.

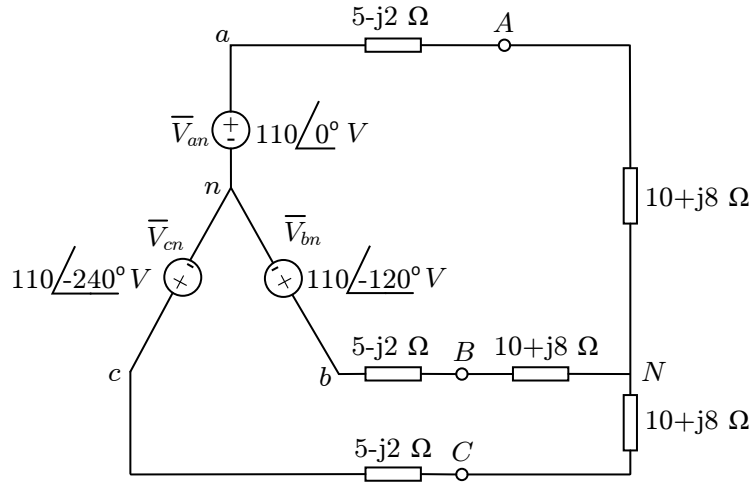


Figure 11 Three-wire  $Y - Y$  system.

### Solution

Note:  $\overline{bar}$  indicates phasor quantity.

The three-phase circuit in Figure 11 is balanced. We may replace it with its single-phase equivalent circuit.

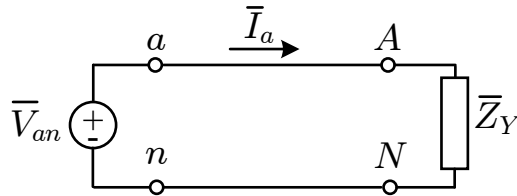


Figure 12 Single-phase equivalent circuit.

We obtain  $\overline{I}_a$  from the single-phase analysis as

$$\overline{I}_a = \frac{\overline{V}_{an}}{\overline{Z}_Y}$$

where,  $\overline{Z}_Y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155/21.8^\circ$ . Hence,

$$\overline{I}_a = \frac{110/0^\circ}{16.155/21.8^\circ} = 6.81/-21.8^\circ \text{ A}$$

Since the source voltages in Figure 11 are in positive sequence, the line currents are also in positive sequence.

$$\overline{I}_b = \overline{I}_a/-120^\circ = 6.81/-141.8^\circ \text{ A}$$

$$\overline{I}_c = \overline{I}_a/-240^\circ = 6.81/-261.8^\circ = 6.81/98.2^\circ \text{ A}$$

5. A balanced  $abc$ -sequence  $Y$ -connected source with  $|\bar{V}_{an}| = 100 \text{ V}$  is connected to a  $\Delta$ -connected balanced load  $(8 + j4) \Omega$  per phase as shown in Figure 13. Calculate the phase and line currents.

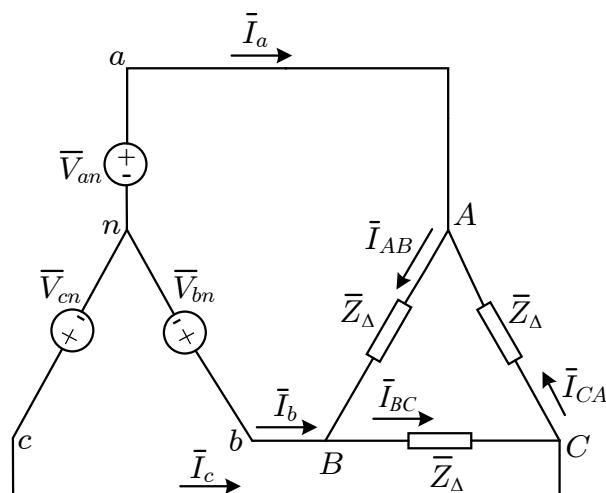


Figure 13 Three-wire  $Y - \Delta$  system.

### Solution

#### METHOD 1:

The load impedance is

$$\bar{Z}_{\Delta} = 8 + j4 = 8.944/26.57^{\circ} \Omega$$

If the phase voltage  $\bar{V}_{an} = 100/10^{\circ}$ , then the line voltage is

$$\bar{V}_{ab} = \sqrt{3}\bar{V}_{an}/30^{\circ} = 100\sqrt{3}/10^{\circ} + 30^{\circ} = \bar{V}_{AB}$$

or,

$$\bar{V}_{AB} = 173.2/40^{\circ}$$

The phase currents are

$$\begin{aligned}\bar{I}_{AB} &= \frac{\bar{V}_{AB}}{\bar{Z}_{\Delta}} = \frac{173.2/40^{\circ}}{8.944/26.57^{\circ}} = 19.36/13.43^{\circ} \text{ A} \\ \bar{I}_{BC} &= \bar{I}_{AB}/-120^{\circ} = 19.36/-106.57^{\circ} \text{ A} \\ \bar{I}_{CA} &= \bar{I}_{AB}/+120^{\circ} = 19.36/133.43^{\circ} \text{ A}\end{aligned}$$

The line currents are

$$\begin{aligned}\bar{I}_a &= \sqrt{3}\bar{I}_{AB}/-30^{\circ} = \sqrt{3}(19.36)/13.43^{\circ} - 30^{\circ} = 33.53/-16.57^{\circ} \text{ A} \\ \bar{I}_b &= \bar{I}_a/-120^{\circ} = 33.53/-136.57^{\circ} \text{ A} \\ \bar{I}_c &= \bar{I}_a/+120^{\circ} = 33.53/103.43^{\circ} \text{ A}\end{aligned}$$

#### METHOD 2:

Alternatively, using single-phase analysis,

$$\bar{I}_a = \frac{\bar{V}_{an}}{\frac{\bar{Z}_{\Delta}}{3}} = \frac{100/10^{\circ}}{2.981/26.57^{\circ}} = 33.54/-16.57^{\circ} \text{ A}$$

Other line currents are obtained using the  $abc$  phase sequence as above.

---

That's it.